

**EHB205 Introduction to Logic Design
2nd Homework**

a ₁	a ₀	b ₁	b ₀	c ₂	c ₁	c ₀
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Boolean functions for the outputs $c_2(a_1, a_0, b_1, b_0)$, $c_1(a_1, a_0, b_1, b_0)$ and $c_0(a_1, a_0, b_1, b_0)$ shown by the above truth table will be implemented.

- 1) Create a new project as explained in your first homework.
- 2) Take "OR_gate.vhd" and "OR_gate_tb.vhd" files from Ninova. You will design your circuit by changing these files. Save these files by giving proper names that represent your two different designs described below.
- 3) Add your "*.vhd" by "Add Sources", "Add or create design sources" to your project.
- 4) Add your "*_tb.vhd" by "Add Sources", "Add or create simulation sources" to your project.
- 5) Change the number of inputs and outputs according to your circuit.
- 6) Change the data types of inputs and outputs according to the examples given in

http://www.csit-sun.pub.ro/courses/Masterat/Materiale_Suplimentare/Xilinx%20Synthesis%20Technology/toolbox.xilinx.com/docsan/xilinx4/data/docs/xst/vhdl3.html
<https://startingelectronics.org/software/VHDL-CPLD-course/tut13-VHDL-data-types-and-operators/>
<http://www.brunel.ac.uk/~eestmba/hdl/dtypevhdl1.html>
https://en.wikibooks.org/wiki/Programmable_Logic/VHDL_Data_Types
<https://web.engr.oregonstate.edu/~sllu/vhdl/lec2e.html>

- 7) Describe the functionality of your circuit under "architecture" by using "case statement" as given in the following web pages

<https://www.ics.uci.edu/~jmoorkan/vhdlref/cases.html>
<https://www.nandland.com/vhdl/examples/example-case-statement.html>
<https://www.allaboutcircuits.com/technical-articles/sequential-vhdl-if-and-case-statements/>
<http://vhdl.renerta.com/mobile/source/vhd00014.htm>
<https://insights.sigasi.com/tech/signal-assignments-vhdl-withselect-whenelse-and-case/>

- 8) Make sure that “*.vhd” is your top module. You can change top module by right clicking to the module that you would like to implement and choose “Set as Top” from the list. Produce the RTL schematic of your design.
- 9) Write the test bench file to test your design by using “*_tb.vhd”. Simulate your design.
- 10) Simplify the $c_2(a_1, a_0, b_1, b_0)$, $c_1(a_1, a_0, b_1, b_0)$ and $c_0(a_1, a_0, b_1, b_0)$ functions.
- 11) Add your second “*.vhd” to your project. Describe the functionality of your circuit under “architecture begin” by using “data flow modelling” as given in the following web pages

<https://vhdlguide.readthedocs.io/en/latest/vhdl/dataflow.html>
<https://www.oreilly.com/library/view/vhdl/9788131732113/xhtml/chapter005.xhtml>
<https://buzztech.in/vhdl-modelling-styles-behavioral-dataflow-structural/>
<https://www.technobyte.org/vhdl-code-for-an-encoder-dataflow/>

- 12) Make sure that your second “*.vhd” is your top module. Produce the RTL schematic of your design.
- 13) Write the test bench file to test your design by using your second “*_tb.vhd”. Simulate your design.

References

- 1) Frank Vahid, **Digital design, with RTL design, VHDL, and Verilog**, Hoboken, NJ : John Wiley, 2010
- 2) Peter D Minns, **FSM-based digital design using Verilog HDL**, Chichester, England : J. Wiley & Sons , c2008
- 3) Pong P. Chu, **FPGA prototyping by Verilog examples Xilinx Spartan -3 version**, Hoboken, N.J. : J. Wiley & Sons, c2008